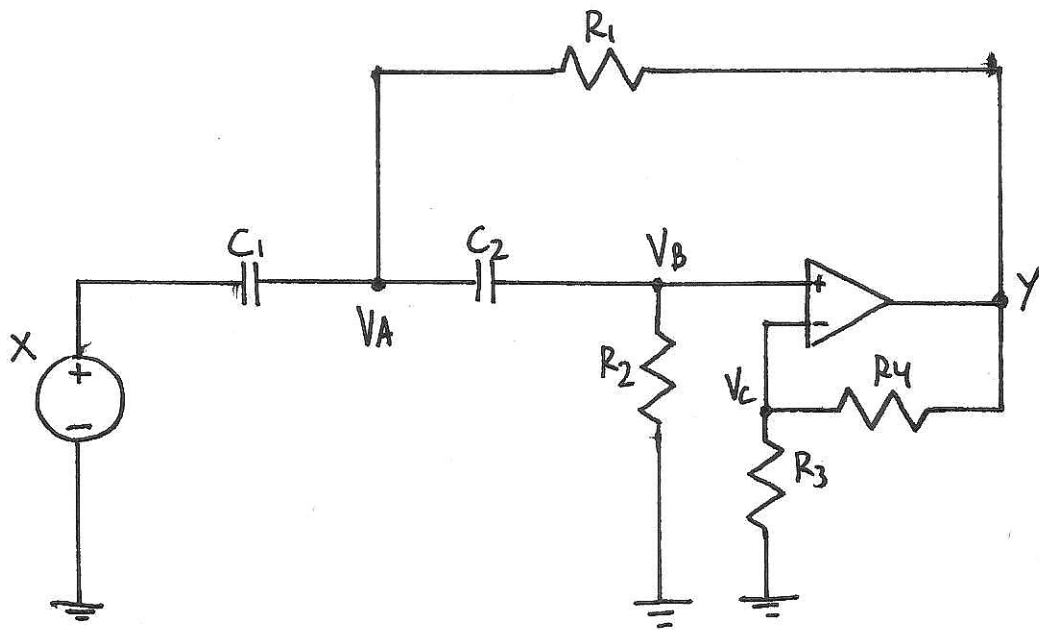


# SIGNALS AND SYSTEMS - WEEK 6



Problem 1

Derive the frequency characteristic  $H(\omega)$ .

Sol

Replace capacitors with their impedance  $Z_c = \frac{1}{j\omega C}$ , because then we can use Ohm's law  $I = \frac{V}{Z}$ .

$$\frac{V_A - X}{Z_{C1}} + \frac{V_A - V_B}{Z_{C2}} + \frac{V_A - Y}{R_1} = 0$$

$$\frac{V_B - V_A}{Z_{C2}} + \frac{V_B}{R_2} = 0$$

Insert  $Z_c = \frac{1}{j\omega C}$ .

$$(V_A - X)j\omega C_1 + (V_A - V_B)j\omega C_2 + \frac{V_A - Y}{R_1} = 0$$

$$(V_B - V_A)j\omega C_2 + \frac{V_B}{R_2} = 0$$

Constraint:  $V_B = V_C = \frac{Y}{K}$ ,  $K = 1 + \frac{R_4}{R_3}$ .

$$\text{Solving in Maple yields: } H(\omega) = \frac{Y}{X} = \frac{K \cdot (j\omega)^2}{(j\omega)^2 + j\omega \left( \frac{1}{R_2 C_1} + \frac{1}{R_2 C_2} + \frac{1-K}{R_1 C_1} \right) + \frac{1}{R_1 R_2 C_1 C_2}}$$

## Problem 2

Derive the differential equation.

Sol

$$H(\omega) = \frac{k \cdot (j\omega)^2}{(j\omega)^2 + j\omega \left( \frac{1}{R_2 C_1} + \frac{1}{R_2 C_2} + \frac{1-k}{R_1 C_1} \right) + \frac{1}{R_1 R_2 C_1 C_2}} = \frac{Y}{X}$$

$$Y(\omega) \cdot \left[ (j\omega)^2 + j\omega \left( \frac{1}{R_2 C_1} + \frac{1}{R_2 C_2} + \frac{1-k}{R_1 C_1} \right) + \frac{1}{R_1 R_2 C_1 C_2} \right] = X(\omega) k (j\omega)^2$$

This equation is in the frequency domain.

To obtain the differential equation, transform back to time.

Time  $\leftrightarrow$  Frequency

$$\frac{d}{dt} \leftrightarrow j\omega$$

$$Y(t) \left[ D^2 + D \left( \frac{1}{R_2 C_1} + \frac{1}{R_2 C_2} + \frac{1-k}{R_1 C_1} \right) + \frac{1}{R_1 R_2 C_1 C_2} \right] = X(t) D^2 \cdot k$$

$$\ddot{Y}(t) + \dot{Y}(t) \left( \frac{1}{R_2 C_1} + \frac{1}{R_2 C_2} + \frac{1-k}{R_1 C_1} \right) + \frac{Y(t)}{R_1 R_2 C_1 C_2} = k \ddot{X}(t)$$

Conclusion:

It is easy to find the differential equation via the transfer function,  $H(\omega)$ .

### Problem 3

Determine passband gain and stopband asymptote slope.

Sol

The numerical transfer function is obtained by inserting component values:

$$H(\omega) = \frac{2(j\omega)^2}{(j\omega)^2 + 0.6283j\omega + 0.0987}$$

It's a highpass filter, so passband lies in the high frequencies

$$\text{Passband gain: } |H(10^{12})| = 2 = 6 \text{ dB} \quad (K=2)$$

The stopband lies in the low frequencies:

Stopband slope: ~~20 dB/dec~~

$$\begin{aligned} 20 \log_{10}(|H(10^5)|) - 20 \log_{10}(|H(10^{-6})|) \\ = 40 \frac{\text{dB}}{\text{dec}} \end{aligned}$$

Because it's a  $n=2$  order highpass filter, the slope is

$$n \cdot 20 \frac{\text{dB}}{\text{dec}} = 40 \frac{\text{dB}}{\text{dec}}$$

### Problem 4

Find phase angle at low and high frequencies.

Sol



$$\bullet \text{ Argument}(H(0)) = 180^\circ$$

$$\bullet \text{ Argument}(H(10^{12})) = 0$$

## Problem 5

Plot the amplitude and phase characteristic.

Sol

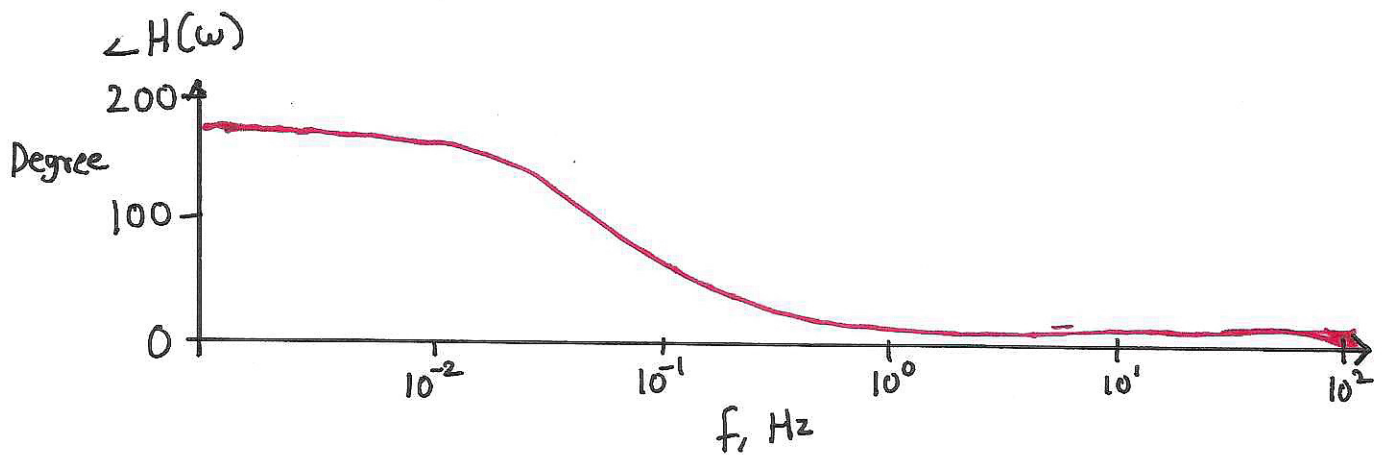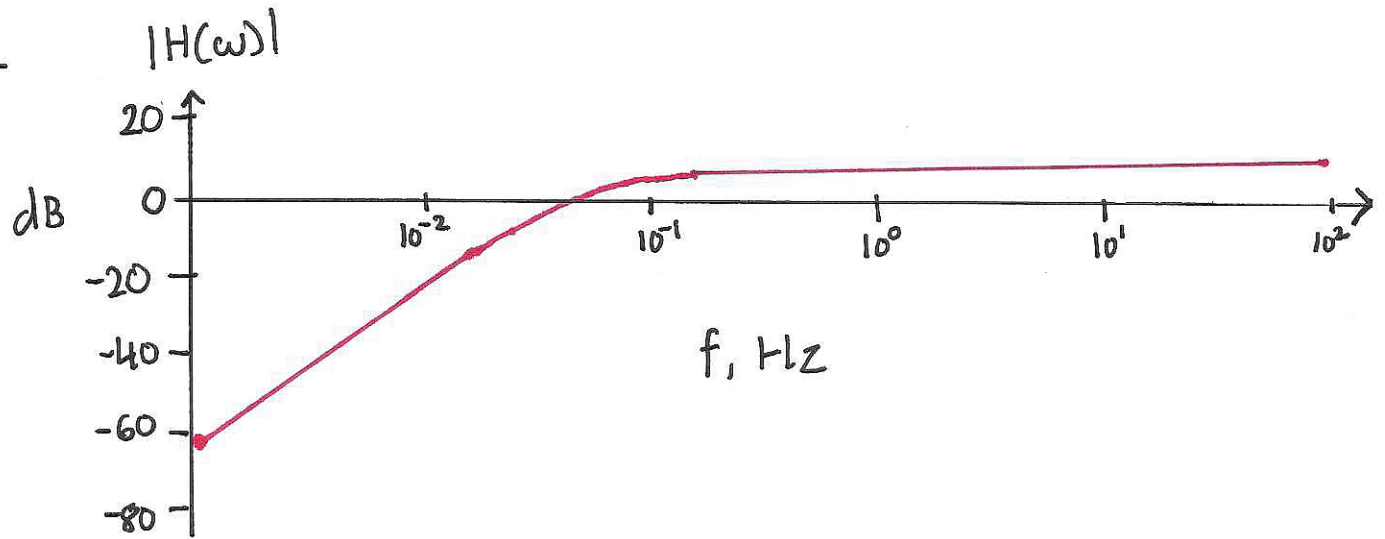

Low frequency

$$|H(\omega)| = -\infty$$

$$\angle H(\omega) = 180^\circ$$

High frequency

$$|H(\omega)| = k$$

$$\angle H(\omega) = 0^\circ$$

For 2nd order Sallen-key highpass filter.