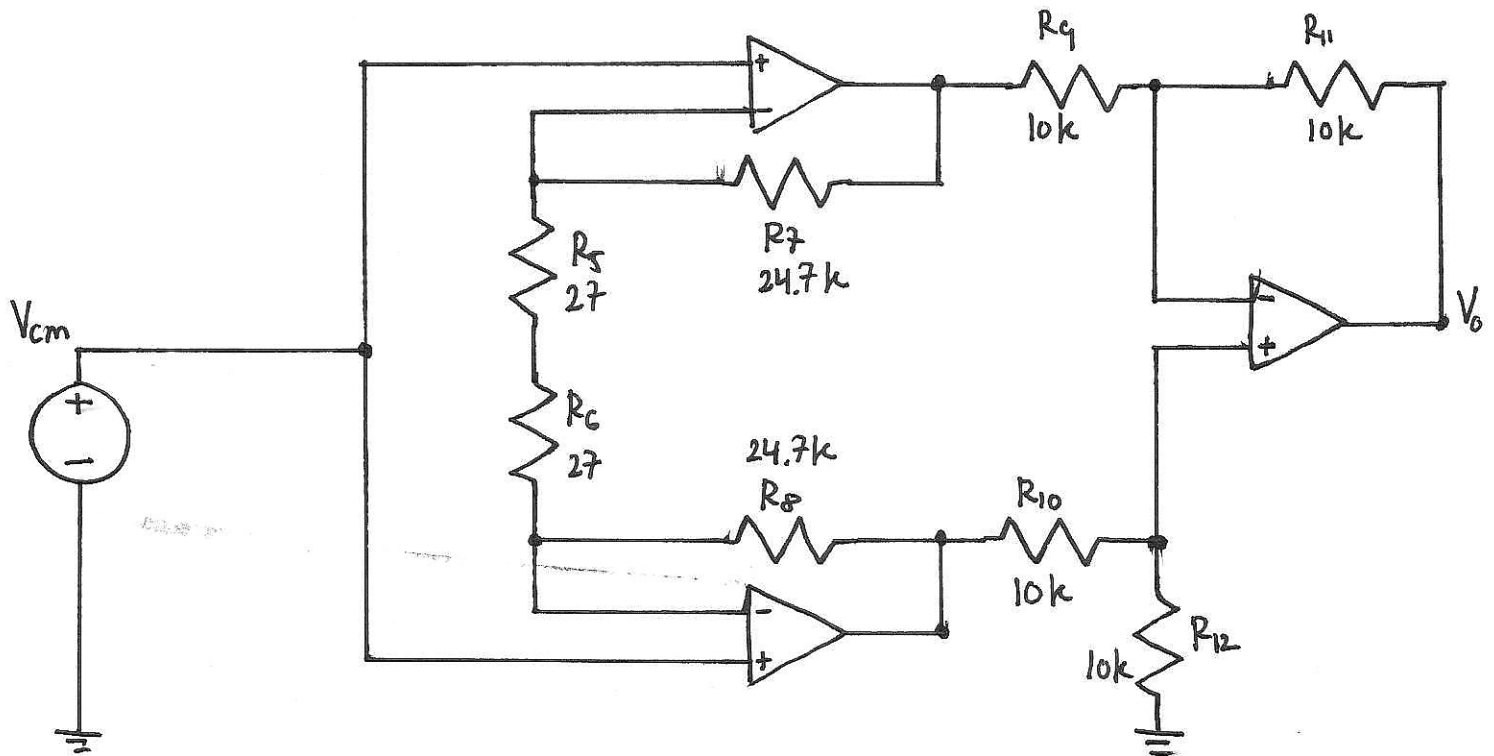


SIGNALS AND SYSTEMS - WEEK 7


Problem 1

Calculate the common mode gain G_c , and CMRR.



Sol

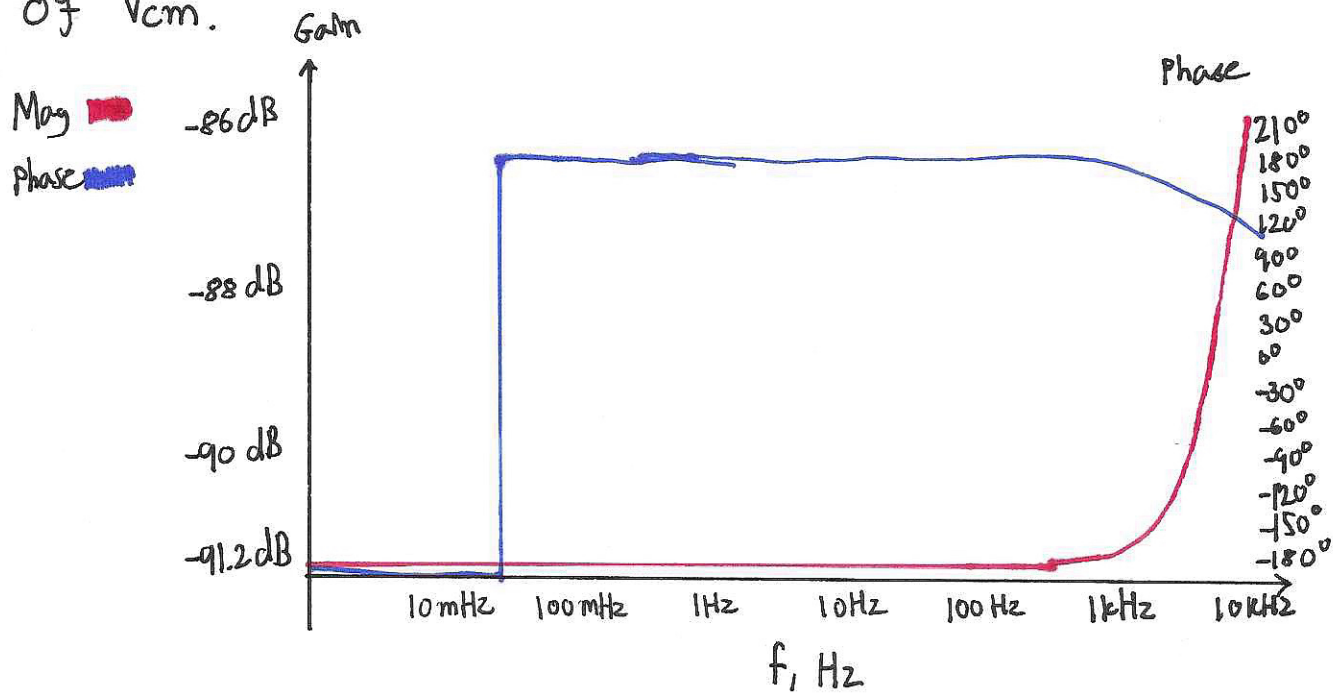Common mode gain G_c can be found with an ac sweep of V_{cm} .



Observe that $\left| \frac{V_o}{V_{cm}} \right| = |G_c| = -91.2 \text{ dB}$

So, a common mode voltage gets attenuated by 91.2 dB.

$$\text{CMRR} = \frac{|G_d|}{|G_c|}$$

$$|G_d| = 1 + \frac{49.4 \text{ k}\Omega}{R_G} = 1 + \frac{49.4 \text{ k}\Omega}{54 \Omega} = 916 = 59 \text{ dB}$$

$$\text{CMRR} = G_{d, \text{dB}} - G_{c, \text{dB}} = 59 \text{ dB} - (-91.2 \text{ dB})$$

$$\text{CMRR} = 150 \text{ dB} \quad (\text{very good})$$

Example

Given this setting

- $V_{cm} = 2 \text{ V}$
- $V_d = 5 \text{ mV}$

how much CMRR is needed if on the output of the in-amp want $V_{cm,o} = 2 \text{ mV}$ and $V_{d,o} = 5 \text{ V}$?

Sol

$$\text{Common mode gain: } \frac{V_{cm,o}}{V_{cm}} = \frac{2 \text{ mV}}{2 \text{ V}} = \frac{1}{1000} = -60 \text{ dB}$$

$$\text{Differential gain: } \frac{V_{d,o}}{V_d} = \frac{5 \text{ V}}{5 \text{ mV}} = 1000 = 60 \text{ dB}$$

Our in-amp needs at least $\text{CMRR} = 60 \text{ dB} - (-60 \text{ dB}) = 120 \text{ dB}$ to fulfill requirements.


Problem 2

Create an imbalance (asymmetry) in the in-amp by setting $R_{11} = 11 \text{ k}\Omega$.

What is CMRR now?

Sol

We plot the frequency characteristic $\frac{V_o}{V_{cm}}$ again to find $|G_c|$.

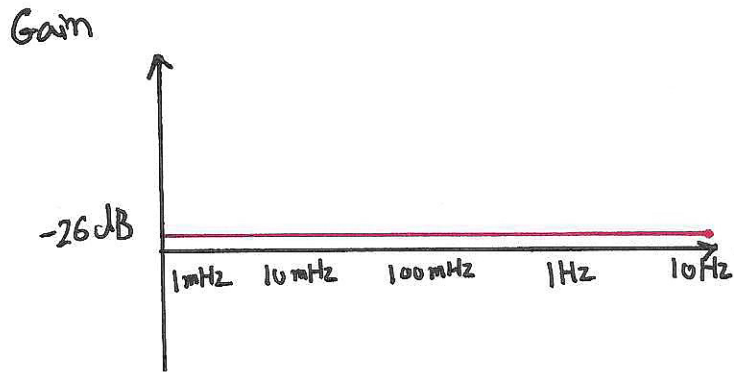

$$|G_c| = -26 \text{ dB}$$

$$|G_d| = 59 \text{ dB}$$

$$\text{CMRR} = 59 \text{ dB} - (-26 \text{ dB}) = 85 \text{ dB} \quad (\text{pretty bad})$$

Observation:

It's very important for in-amps to have perfect symmetry, because imbalance lowers the CMRR significantly.


Problem 3

Set both half-cell batteries to $V_{HC} = 223 \text{ mV}$.

Then, set one to 100 mV , the other to 223 mV .

What will be the output?

Sol

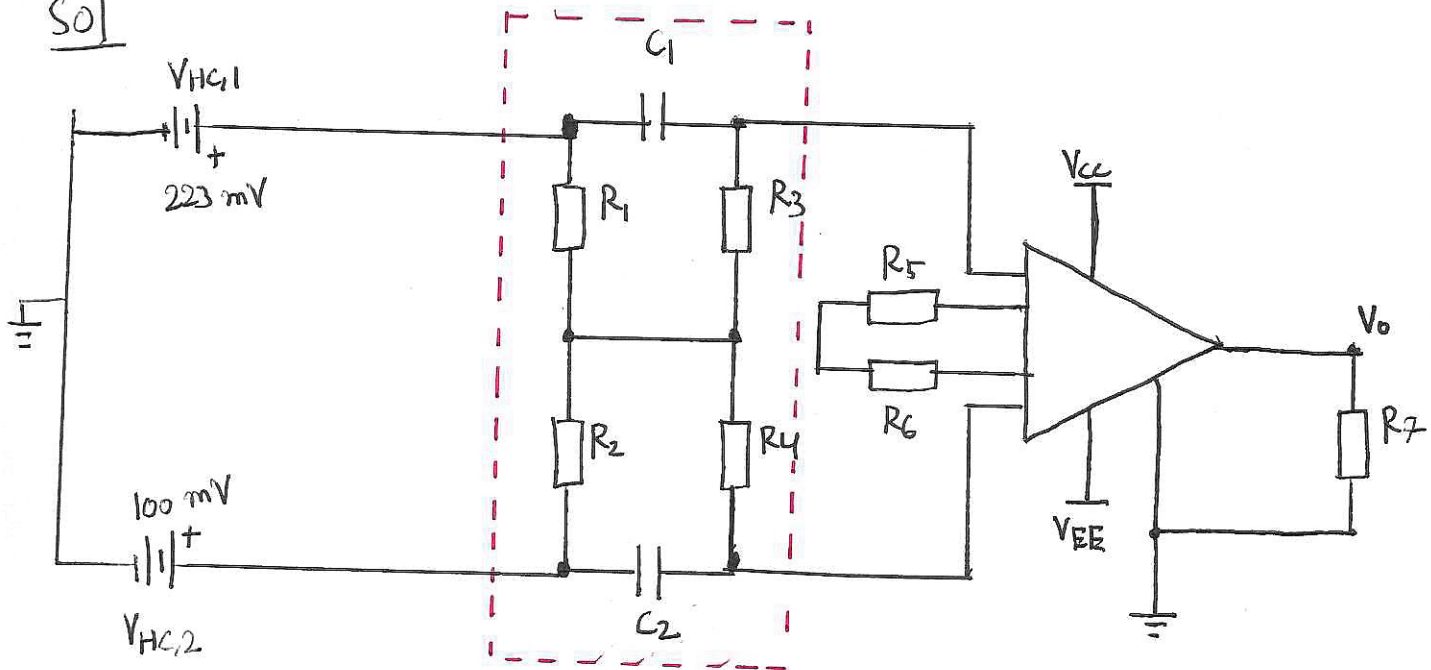

Highpass filter

Due to the highpass filter, any DC-voltage will be filtered away and not appear on the in-amp's input terminals.

So, we expect $V_o = 0 \text{ V}$ in this case, regardless of if $V_{HC,1}$ and $V_{HC,2}$ are different.


Some offset voltage (-44 mV) may appear at V_o , but this is caused by the in-amp itself.

Problem 4

Apply two differential voltages $\frac{V_d}{2} = 2.5 \text{ mV}$ with $f = 10 \text{ Hz}$.

What will the output be?

Sol

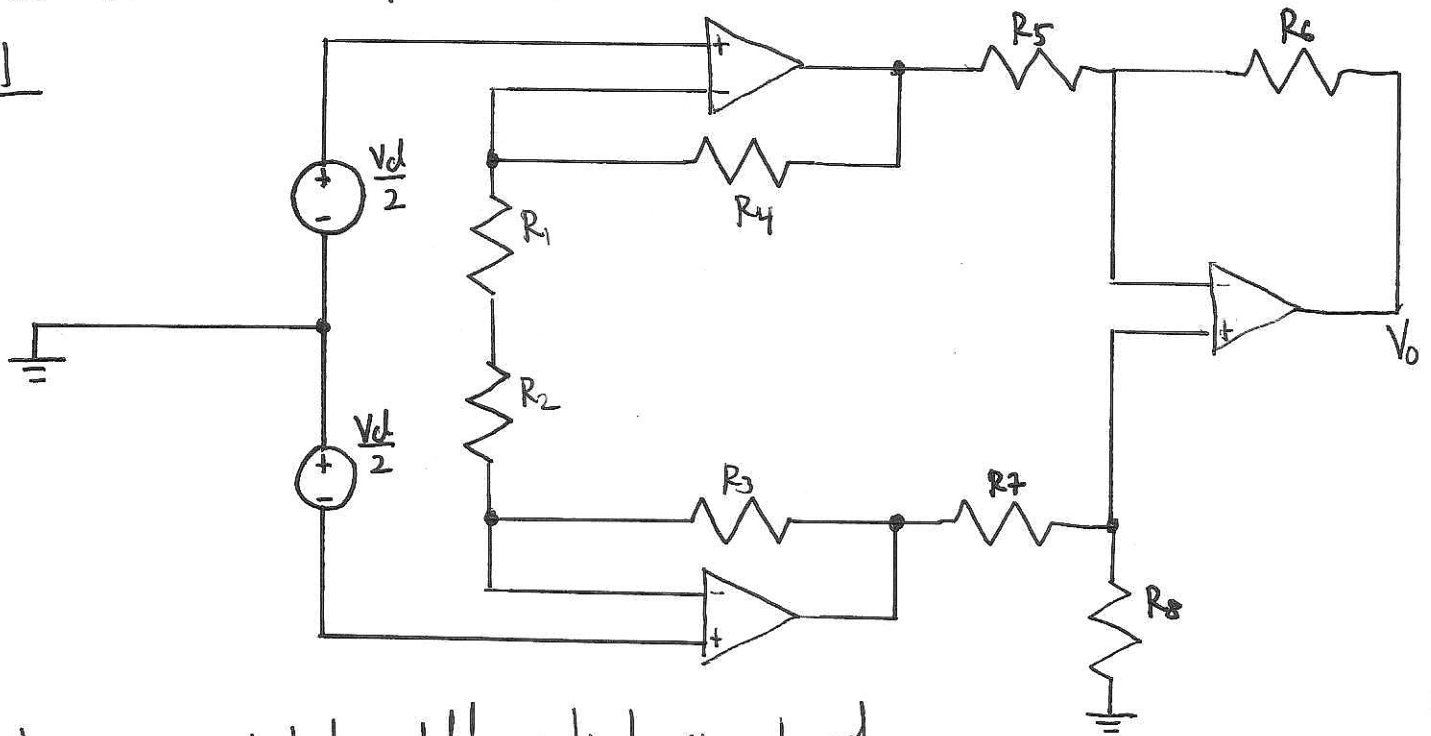


We have a total differential signal of

$$V_d = 5 \text{ mV} \cdot \sin(2\pi \cdot 10 \text{ Hz})$$

We expect an output voltage

$$V_o = V_d \cdot G_d = 4.58 \cdot \sin(2\pi \cdot 10 \text{ Hz})$$

With $V_{pp} = 9.16 \text{ V}$.

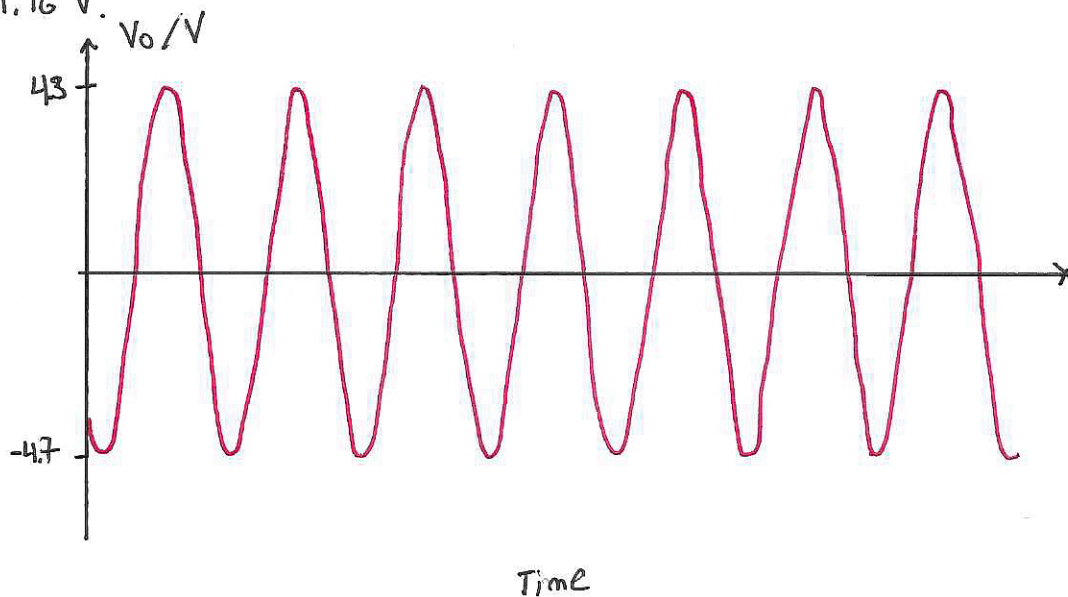

$V_{pp} = 4.3 \text{ V} - (-4.7) = 9 \text{ V}$ matches almost expectation.

Any DC-offset will be highpass filtered.

Problem 5

Does changing the highpass filter components affect the DC-voltage attenuation?

Sol


No.

The component values only affect cutoff frequency.

However, any highpass filter provides ∞ DC voltage attenuation.

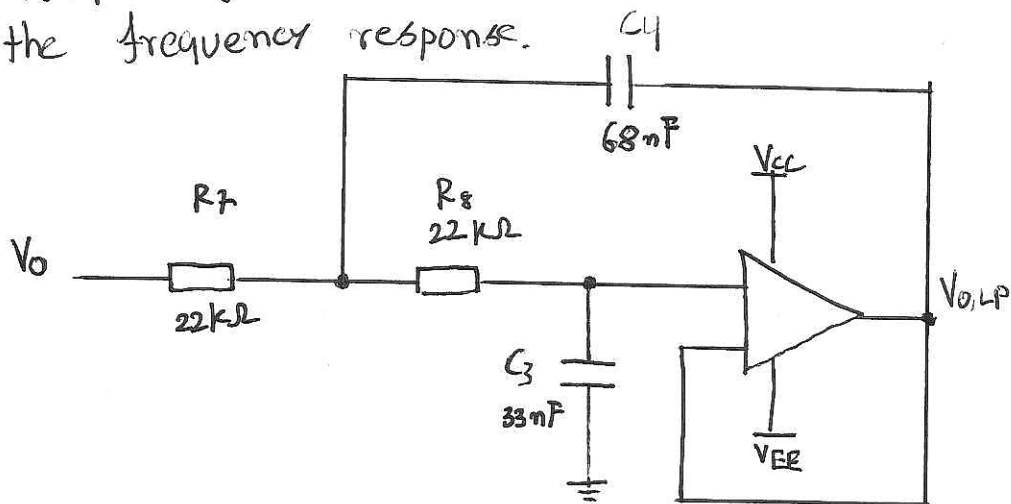Problem 6

Cascade a lowpass filter after the in-amp and see how it affects the frequency response.




Sol

The lowpass should attenuate high frequent signals.

V_o █

$V_{o,LP}$ █

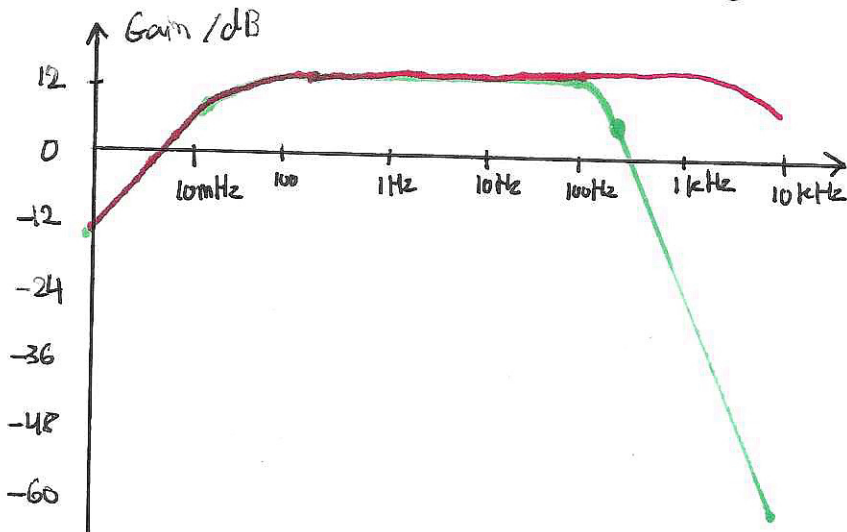


$$\left. \begin{array}{l} |V_{o,LP}(10\text{ Hz})| = 13\text{ dB} \\ |V_{o,LP}(1\text{ kHz})| = -20\text{ dB} \end{array} \right\} \frac{|V_{o,LP}(1\text{ kHz})|}{|V_{o,LP}(10\text{ Hz})|} = -20\text{ dB} - 13\text{ dB} = -33\text{ dB}$$

Problem 7

To make sure $V_o \in [0, 5 \text{ V}]$ a gain stage and offset stage can be used in extension to the L_p -filter.

Find max gain and offset.

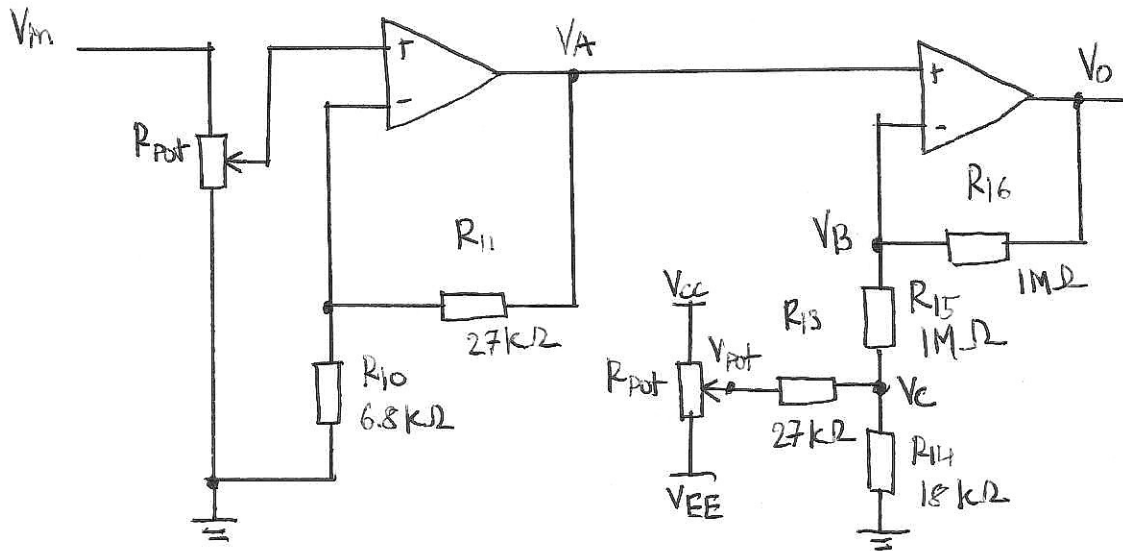

Sol

Call wiper position of first potentiometer $\alpha \in [0, 1]$.

$$V_A = \alpha V_{in} \left(1 + \frac{R_{11}}{R_{10}} \right)$$

Write node equations for V_B and V_c .

$$\frac{V_B - V_o}{R_{16}} + \frac{V_B - V_c}{R_{15}} = 0$$

$$\frac{V_c - V_B}{R_{15}} + \frac{V_c - V_{pot}}{R_{13}} + \frac{V_c}{R_{14}} = 0$$

Constraint! $V_B = V_A$.

Inserting values and solving for V_o, V_c yields:

$$V_o = \underbrace{\alpha V_{in} \cdot 9.88}_{\text{Gain}} - \underbrace{0.395 V_{pot}}_{\text{offset}}, \quad V_{pot} \in [-9 \text{ V}, 9 \text{ V}]$$

Max: Gain = 9.88 \approx 10, offset = $\pm 3.56 \text{ V}$