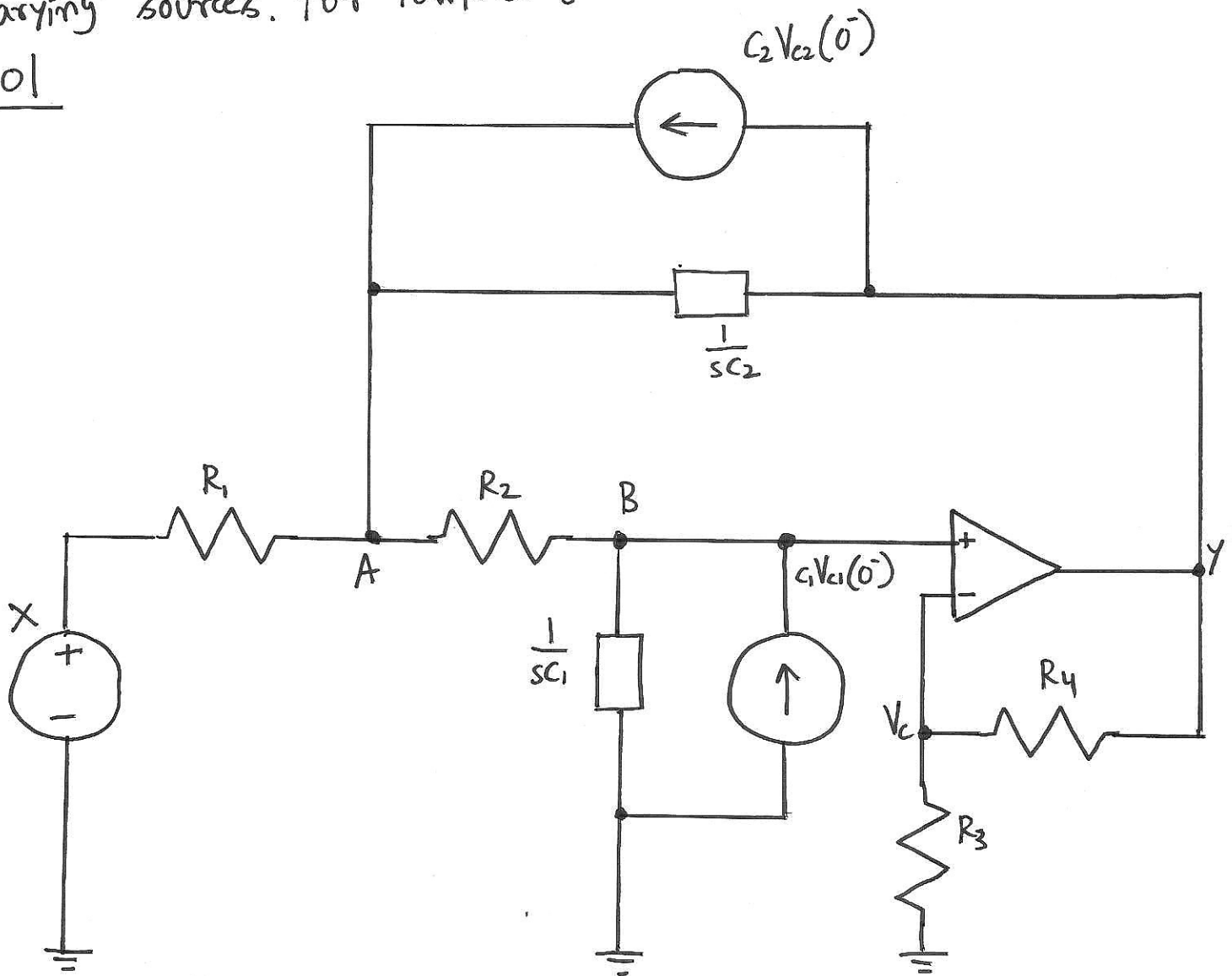


# SIGNALS AND SYSTEMS - WEEK 9

## Problem 1

Laplace transform frequency dependent components and time-varying sources. For lowpass filter.

Sol




Node equations:

$$\frac{V_A - X}{R_1} + \frac{V_A - V_B}{R_2} + (V_A - Y)sC_2 - c_2V_{c_2}(0^-) = 0$$

$$\frac{V_B - V_A}{R_2} + V_B \cdot sC_1 - c_1V_{c_1}(0^-) = 0$$

$$\text{Constraint: } V_B = V_C = \frac{Y}{K}, \quad K = 1 + \frac{R_4}{R_3}$$
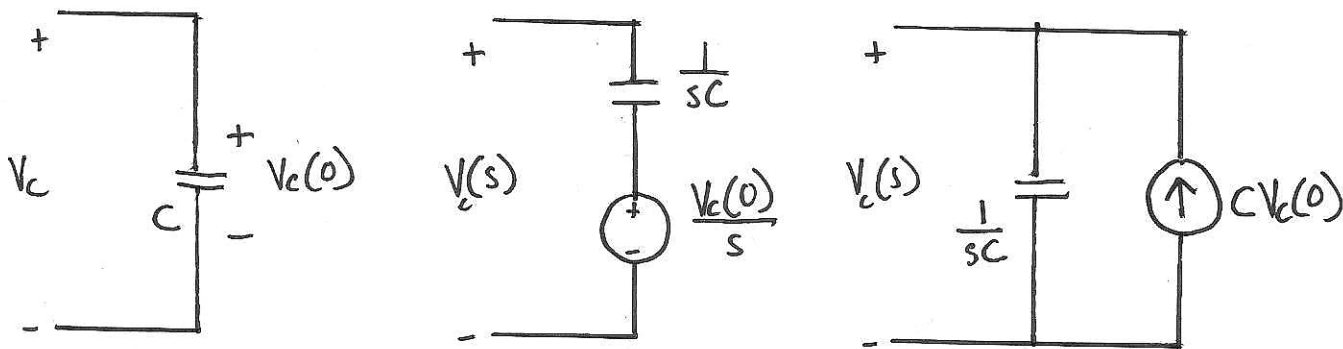
# Laplace transform of capacitor with initial voltage.



Note, current source direction is opposite of polarity.

## Problem 2

Derive the system response  $Y(s) = \frac{P(s)}{Q(s)} X(s) + \frac{I(s)}{Q(s)}$

Sol.

Define the equations in Maple:

$$\text{sys} := \left\{ \frac{V_A - X}{R_1} + \frac{V_A - V_B}{R_2} + sC_2 \cdot (V_A - Y) - C_2 V_{c2}(0^-) = 0, \frac{V_B - V_A}{R_2} + sC_1 \cdot V_B - C_1 V_{c1}(0^-) = 0 \right\}$$

$$V_B := \frac{Y}{K}$$

Solve(sys, {V\_A, V\_B})

$$Y = \frac{k(C_1 C_2 R_1 R_2 V_{c1}(0^-) s + C_1 R_1 V_{c1}(0^-) + C_1 R_2 V_{c1}(0^-) + C_2 R_1 V_{c2}(0^-) + X)}{C_1 C_2 R_1 R_2 s^2 + s(C_1 R_1 + C_1 R_2 + C_2 R_1 - C_2 R_1 k) + 1}$$

Using Maple's collect(%, X) on the fraction yields:

$$Y(s) = \underbrace{\frac{k}{C_1 C_2 R_1 R_2 s^2 + s(C_1 R_1 + C_1 R_2 + C_2 R_1 - C_2 R_1 k) + 1}}_{\text{Zero state response}} X(s) + \underbrace{\frac{k(C_1 C_2 R_1 R_2 V_{c1}(0^-) s + C_1 R_1 V_{c1}(0^-) + C_1 R_2 V_{c1}(0^-) + C_2 R_1 V_{c2}(0^-))}{C_1 C_2 R_1 R_2 s^2 + s(C_1 R_1 + C_1 R_2 + C_2 R_1 - C_2 R_1 k) + 1}}_{\text{Zero input response}}$$

$$Y(s) = \frac{b_0}{s^2 + a_1 s + a_0} X(s) + \frac{k}{C_1 R_2} V_{c2}(0^-) + \frac{k(s + \frac{1}{C_2 R_2} + \frac{1}{C_2 R_1}) V_{c1}(0^-)}{s^2 + a_1 s + a_0}$$

### Problem 3

Solve for the zero-input response using Maple.

$$\frac{\text{Sol}}{Y_{zi}(s)} = \frac{\frac{k}{C_1 R_2} V_{c2}(0^-) + k \left( s + \frac{1}{C_2 R_2} + \frac{1}{C_2 R_1} \right) V_{c1}(0^-)}{s^2 + a_1 s + a_0}$$

$$Y_{zi}(s) = \frac{2.116}{s + 147.306} - \frac{0.116}{s + 2680.2}$$

Inverse Laplace transform to find  $Y_{zi}(t)$ .

$$\mathcal{L}^{-1} \left\{ \frac{2.116}{s + 147.3} - \frac{0.116}{s + 2680.2} \right\} = 2.11e^{-147.3t} - 0.116e^{-2680.2t}$$

↑  
invlaplace

### Problem 4

Solve for the zero-state response, to the input  $2u(t) = x(t)$ .

Sol

$$Y_{zs}(s) = \frac{b_0}{s^2 + a_1 s + a_0} X = \underbrace{\left[ \frac{4}{s} - \frac{4.232}{s + 147.3} + \frac{0.2326}{s + 2680} \right]}_{H(s)} \cdot \underbrace{\frac{2}{s}}_{X(s)}$$

$$\text{invlaplace} \left( \left[ \frac{4}{s} - \frac{4.232}{s + 147.3} + \frac{0.2326}{s + 2680} \right] \cdot \frac{2}{s}, s, t \right)$$

$$Y_{zs}(t) = 4 - 4.232e^{-147.3t} + 0.2326e^{-2680t}$$